

# **CSE260 Lab Report**

**Experiment Name:**

**Parity Generator and Checker**

**Submitted by**

**Name: Tahsin Ashrafee Susmit**

**ID: 20301088**

**Section: 09**

**Date: 18/07/21**

1. Name of the experiment:

Parity Generator and checker

2. Objective:

\* To design and implement on Even parity Generator and Even parity checker using XOR gates. (IC-7486)


3. Required Components and Equipment:

- i. AT -700 Portable Analog/Digital Laboratory
- ii. 7400 x3


In proteus we need:

- i. Logic Probe
- ii. Logic State
- iii. XOR
 
# 4. Experimental Set-up: Even parity Generator:



## Even Parity Checker:

 

5. Results in Tabular form:

For (a) 0111 (b) 1001 (c) 000 (d) 0100, Parity Generation

P	D <sub>3</sub>	D <sub>2</sub>	D <sub>1</sub>	D <sub>0</sub>
1	0	1	1	1
0	1	0	0	1
0	0	0	0	0
1	0	1	0	0

Parity Checker:

P	D <sub>3</sub>	D <sub>2</sub>	D <sub>1</sub>	D <sub>0</sub>	Error
0	1	0	1	0	0
1	1	1	1	0	0
1	1	1	1	1	1
1	0	0	0	0	1

Even Parity generator truth table:

$D_3$	$D_2$	$D_1$	$D_0$	$D_0 \oplus D_1$	$D_2 \oplus D_3$	$(D_0 \oplus D_1) \oplus (D_2 \oplus D_3)$
0	0	0	0	0	0	0
0	0	0	1	1	0	1
0	0	1	0	1	0	1
0	0	1	1	0	0	0
0	1	0	0	0	1	1
0	1	0	1	1	1	0
0	1	1	0	1	1	0
0	1	1	1	0	1	1
1	0	0	0	0	1	1
1	0	0	1	1	1	0
1	0	1	0	1	1	0
1	0	1	1	0	1	1
1	1	0	0	0	0	0
1	1	0	1	1	0	1
1	1	1	0	1	0	1
1	1	1	1	0	0	0



Even parity checker truth table :

P	D <sub>3</sub>	D <sub>2</sub>	D <sub>1</sub>	D <sub>0</sub>	D <sub>0</sub> ⊕ D <sub>1</sub>	D <sub>2</sub> ⊕ D <sub>3</sub>	P ⊕ D <sub>0</sub> ⊕ D <sub>1</sub> ⊕ D <sub>2</sub> ⊕ D <sub>3</sub>	P' ⊕ P
0	0	0	0	0	0	0	0	0
0	0	0	0	1	1	0	1	1
0	0	0	1	0	1	0	1	1
0	0	0	1	1	0	0	0	0
0	0	1	0	0	0	1	1	1
0	0	1	0	1	1	1	0	0
0	0	1	1	0	1	1	0	0
0	0	1	1	1	0	1	1	1
0	1	0	0	0	0	1	1	1
0	1	0	0	1	1	1	0	0
0	1	0	1	0	1	1	0	1
0	1	0	1	1	0	1	1	0
0	1	1	0	0	0	0	0	1
0	1	1	0	1	1	0	1	1
0	1	1	1	0	1	0	1	0
0	1	1	1	1	0	0	0	1
1	0	0	0	0	0	0	0	0
1	0	0	0	1	1	0	1	0
1	0	0	1	0	1	0	1	1
1	0	0	1	1	0	0	0	0
1	0	1	0	0	0	1	1	1
1	0	1	0	1	1	1	0	1
1	0	1	1	0	1	1	0	1
1	0	1	1	1	0	1	1	0
1	1	0	0	0	0	1	1	0
1	1	0	0	1	1	1	0	1
1	1	0	1	0	1	1	0	1
1	1	0	1	1	0	1	1	0
1	1	1	0	0	0	0	0	1
1	1	1	0	1	1	0	1	0
1	1	1	1	0	1	0	1	0
1	1	1	1	1	0	0	0	1

### Discussion :

We know, XOR gate will give output "0" if both the inputs are same. If they are different, the output will be "1". From the truth table of parity generator we can see if the number of "1"s are even output is 0. If we look at the parity checker truth table, if the parity bit matches from the received inputs with its checker, error is "0" else is "1". Thus XOR gates are used to get to the conclusion of error detection.