



LAB-02

CSE251

NAME: MALIHA MEHEJABIN

ID: 20301264

SECTION: 07

GROUP: 01

SEMESTER: FALL'22

DATE OF PERFORMANCE: 16/10/22

DATE OF SUBMISSION: 22/10/22



Title: Study to Half-Wave and Full wave Diode Rectifier Circuit

Theory: The diode rectifier converts the input sinusoidal voltage V_s to a unipolar output V_o ; There are two types of rectifier circuits (i) Half-wave rectifier (ii) Full-wave rectifier

Half-wave Rectifier:

Where only positive half cycle appears at the output and the negative half is blocked, the AC input voltage changes into a unidirectional DC voltage at the output. and the process of removing half of the input signal to establish a dc level is aptly called half-wave rectification.

HW Rectifier with filter capacitor:

Although the rectification stage makes the sine wave voltage to be positive but its result is not flat as DC value. But the capacitor is included to help smooth out the ripples as it wanted.

Peak inverse voltage (PIV):

PIV is the maximum voltage that appears across the diode when it is reverse-biased.

$$PIV = V_m$$

Ripple voltage and Ripple factor:

The output of a rectifier though unidirectional, contains periodically fluctuating components. Value for peak-peak ripple voltage:

$$V_r (p-p) = \frac{V_p}{RCR} = \frac{V_m - V_{D0}}{RCR}$$

Full wave Rectifier / Bridge rectifier :

This rectifier utilizes both halves of the input sinusoid. To provide a unipolar output, it inverts the negative halves of the sine wave.

FW Rectifier with capacitor:

The pulsating nature of the output voltage produced by the rectifier circuits discussed above makes it unsuitable as a dc supply for electronics circuits. A capacitor is placed across load resistor to reduce the variation of output voltage.

Ripple voltage and ripple factor:

value of peak-to-peak ripple voltage,

$$V_{r(p-p)} = \frac{V_p}{2fCR} = \frac{V_m - 2V_{p0}}{2fCR} \quad [\text{for FW rectifier}]$$

[V_p = peak voltage of output ; f = input frequency ; R = resistance]

$$\begin{aligned} \text{ripple factor, } r &= \frac{\text{rms value of alternating components of the output wave}}{\text{average value of the output wave}} \\ &= \frac{V_{r-rms}}{V_{dc}} \end{aligned}$$

Equipments:

- ① p-n junction diode (1N4007) $\times 4$
- ② Resistor ($10k\Omega$) - $\times 1$
- ③ Capacitors ($1\mu F$, $4.7\mu F$) - 1 each
- ④ Function Generator
- ⑤ ~~ss~~ Oscilloscope
- ⑥ Bread board
- ⑦ Chords and wires.

Experimental Observation

1. HW Rectifier without Capacitor:

Peak output voltage, V_p (oscilloscope) = 4.88 V

Average or DC output voltage, V_{dc} (multimeter in DC mode) = 1.513 V

RMS or AC output voltage, V_{r-rms} (multimeter in AC mode) = 1.866 V

2. HW Rectifier with 1 μ F Capacitor:

Peak output voltage, V_p (oscilloscope) = 4.84 V

Peak to peak ripple voltage, $V_{r(p-p)}$ (oscilloscope) = ~~3.451 V~~ 2.56 V

Average or DC value of the ripple voltage, V_{dc} (multimeter in DC mode) = ~~3.451 V~~ 3.451 V

RMS or AC value of the ripple voltage, V_{r-rms} (multimeter in AC mode) = 0.760 V

Ripple factor, $r = V_{r-rms}/V_{dc} = 0.2146$

3. HW Rectifier with 4.7 μ F Capacitor:

Peak output voltage, V_p (oscilloscope) = 4.60 V

Peak to peak ripple voltage, $V_{r(p-p)}$ (oscilloscope) = 1.00 V

Average or DC value of the ripple voltage, V_{dc} (multimeter in DC mode) = 4.27 V

RMS or AC value of the ripple voltage, V_{r-rms} (multimeter in AC mode) = 0.222 V

Ripple factor, $r = V_{r-rms}/V_{dc} = 0.05199$

Theoretical Calculation (Homework)

1. HW Rectifier Without Capacitor:

Peak output voltage, V_p (see the experimental observation) = 5.12 V

Peak input voltage, $V_m = 5.85$

Diode voltage, $V_{D0} = 0.7$ V

DC output voltage of the rectifier, $V_{dc} = \frac{V_m}{\pi} - \frac{V_{D0}}{2} = 1.512$ V

RMS or AC output voltage, $V_{r-rms} = \frac{V_p}{2} = 2.56$ V

2. HW Rectifier With 1 μ F Capacitor:

Peak output voltage, V_p (see the experimental observation) = 4.96 V

Peak to peak ripple voltage, $V_{r(p-p)}$ (see the experimental observation) = 2.64 V

DC value of the ripple voltage, $V_{dc} = V_p - \frac{V_{r(p-p)}}{2} = 3.64$ V

RMS value of the ripple voltage, $V_{r-rms} = \frac{V_{r(p-p)}}{2\sqrt{3}} = 0.762$ V

Ripple factor, $r = V_{r-rms}/V_{dc} = 0.2098$

3. HW Rectifier with 4.7 μ F Capacitor:

Peak output voltage, V_p (see the experimental observation) = 4.88 V

Peak to peak ripple voltage, $V_{r(p-p)}$ (see the experimental observation) = 0.88 V

DC value of the ripple voltage, $V_{dc} = V_p - \frac{V_{r(p-p)}}{2} = 4.44$ V

RMS value of the ripple voltage, $V_{r-rms} = \frac{V_{r(p-p)}}{2\sqrt{3}} = 0.254$ V

Ripple factor, $r = V_{r-rms}/V_{dc} = 0.057$

7. Also measure V_o with a multimeter in dc and ac mode and calculate the ripple factor.
8. Replace $1\mu\text{F}$ Capacitor with $4.7\mu\text{F}$ and repeat steps 4-7.

Experimental Observation

1. FW Rectifier without Capacitor:

Peak output voltage, V_p (oscilloscope) = 4.48V
 Average or DC output voltage, V_{dc} (multimeter in DC mode) = 2.267V
 RMS or AC output voltage, V_{r-rms} (multimeter in AC mode) = 1.374V

2. FW Rectifier with $1\mu\text{F}$ Capacitor:

Peak output voltage, V_p (oscilloscope) = 4.34V
 Peak to peak ripple voltage, $V_{r(p-p)}$ (oscilloscope) = 1.68V
 Average or DC value of the ripple voltage, V_{dc} (multimeter in DC mode) = 3.376V
 RMS or AC value of the ripple voltage, V_{r-rms} (multimeter in AC mode) = 0.401V
 Ripple factor, $r = V_{r-rms}/V_{dc} = 0.11877$

3. FW Rectifier with $4.7\mu\text{F}$ Capacitor:

Peak output voltage, V_p (oscilloscope) = 4.05V
 Peak to peak ripple voltage, $V_{r(p-p)}$ (oscilloscope) = 78
 Average or DC value of the ripple voltage, V_{dc} (multimeter in DC mode) = 3.75V
 RMS or AC value of the ripple voltage, V_{r-rms} (multimeter in AC mode) = 0.187V
 Ripple factor, $r = V_{r-rms}/V_{dc} = 0.048$

Theoretical Calculation (Homework)

1. FW Rectifier without Capacitor:

Peak output voltage, V_p (see the experimental observation) = 4.48V
 Peak input voltage, $V_m = 5.85\text{V}$
 Diode voltage, $V_{D0} = 0.7\text{V}$
 DC output voltage of the rectifier, $V_{dc} = \frac{2V_m}{\pi} - 2V_{D0} = 2.324\text{V}$
 RMS or AC output voltage, $V_{r-rms} = \frac{V_p}{\sqrt{2}} = 3.168\text{V}$

2. FW Rectifier with $1\mu\text{F}$ Capacitor:

Peak output voltage, V_p (see the experimental observation) = 4.44V
 Peak to peak ripple voltage, $V_{r(p-p)}$ (see the experimental observation) = 1.32V
 DC value of the ripple voltage, $V_{dc} = V_p - \frac{V_{r(p-p)}}{2} = 3.78\text{V}$
 RMS value of the ripple voltage, $V_{r-rms} = \frac{V_{r(p-p)}}{2\sqrt{3}} = 0.38\text{V}$
 Ripple factor, $r = V_{r-rms}/V_{dc} = 0.100\text{V}$

3. FW Rectifier with $4.7\mu\text{F}$ Capacitor:


Peak output voltage, V_p (see the experimental observation) = 4.28V
 Peak to peak ripple voltage, V_p (see the experimental observation) = 0.44V
 DC value of the ripple voltage, $V_{dc} = V_p - \frac{V_{r(p-p)}}{2} = 4.06\text{V}$
 RMS value of the ripple voltage, $V_{r-rms} = \frac{V_{r(p-p)}}{2\sqrt{3}} = 0.127\text{V}$
 Ripple factor, $r = V_{r-rms}/V_{dc} = 0.03$

Table:


		Experimental observation			Theoretical calculation		
	C(MF)	V _{r-rms} (V)	V _{dc} (V)	Ripple factor	V _{r-rms} (V)	V _{dc} (V)	Ripple factor
HW	1	0.760	3.451	0.2146	0.762	3.64	0.209
	4.7	0.222	4.27	0.05199	0.254	4.44	0.057
FW	1	0.401	3.376	0.11877	0.38	3.78	0.100
	4.7	0.187	3.75	0.048	0.127	4.06	0.03



Circuit diagrams:



(I) Half-wave rectifier

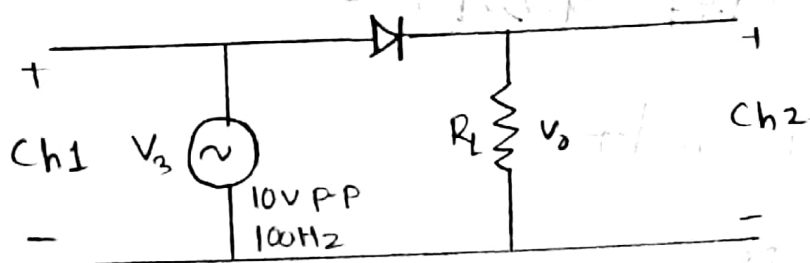

(II) Full wave rectifier

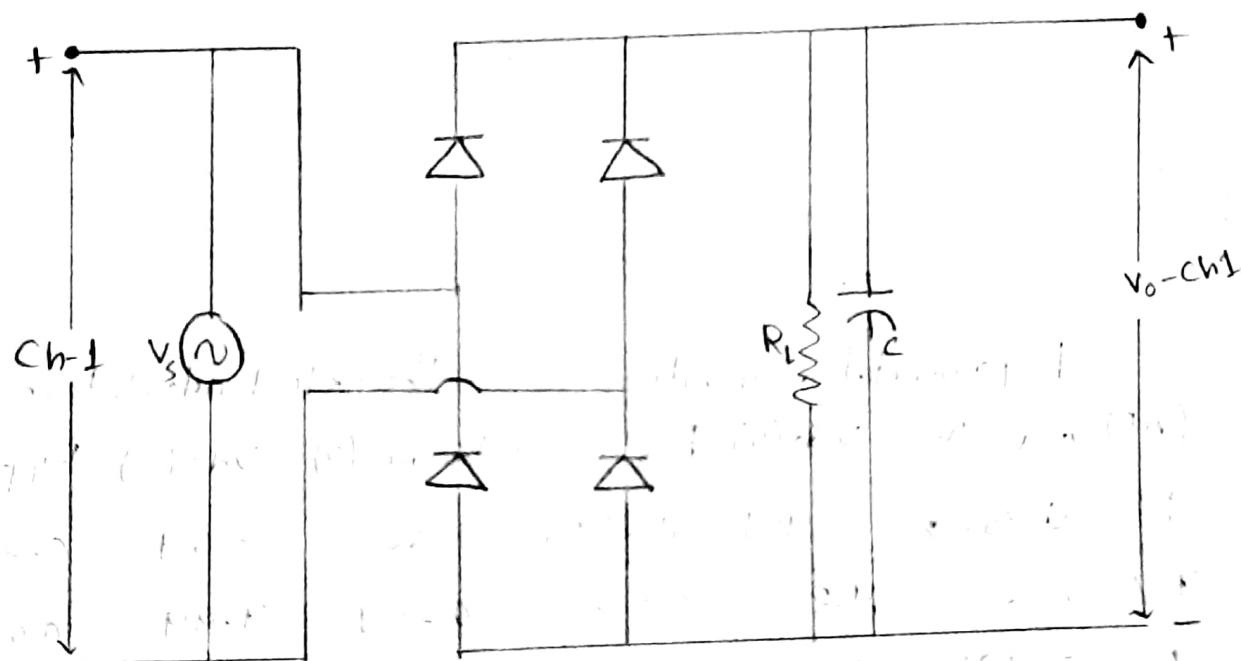

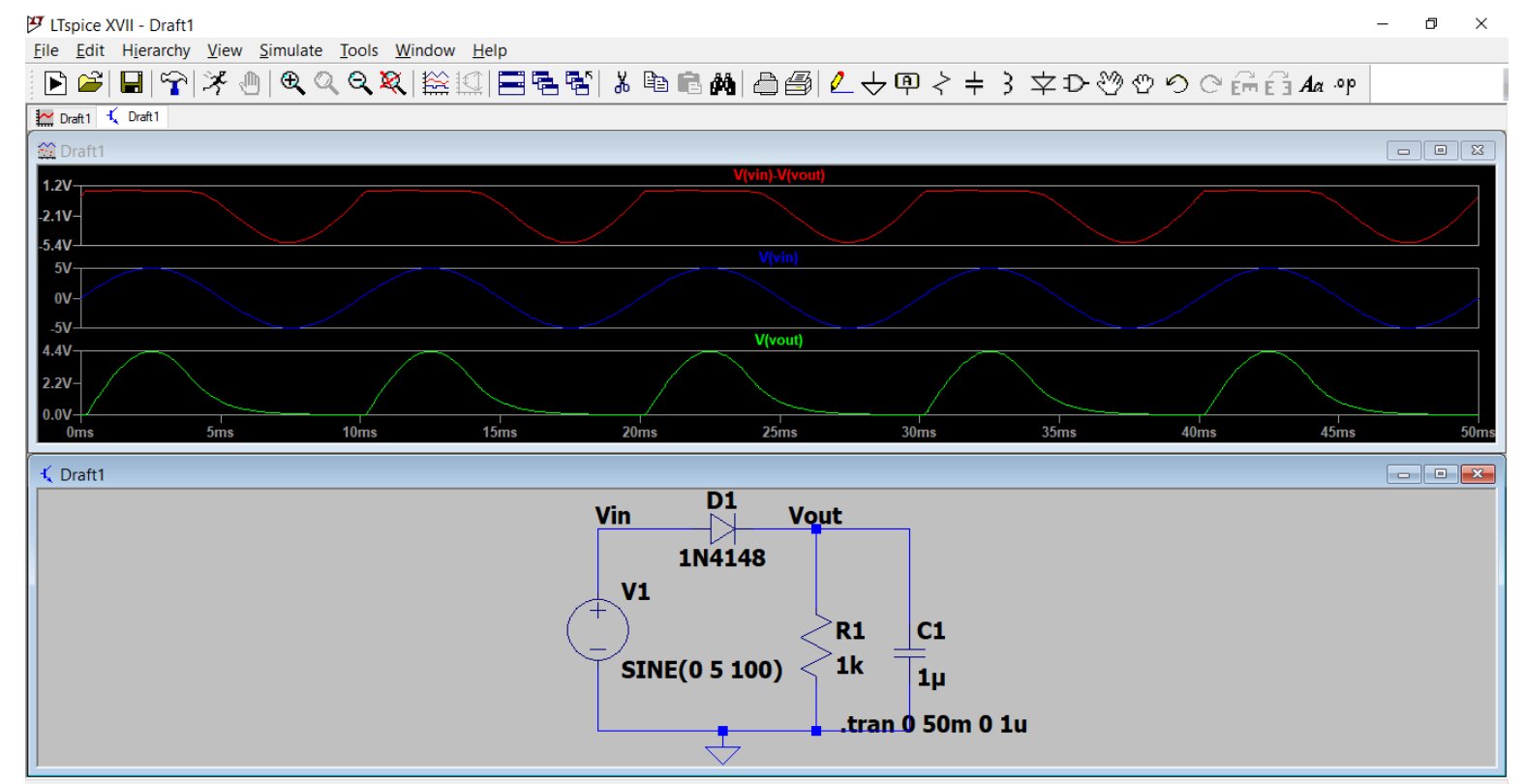
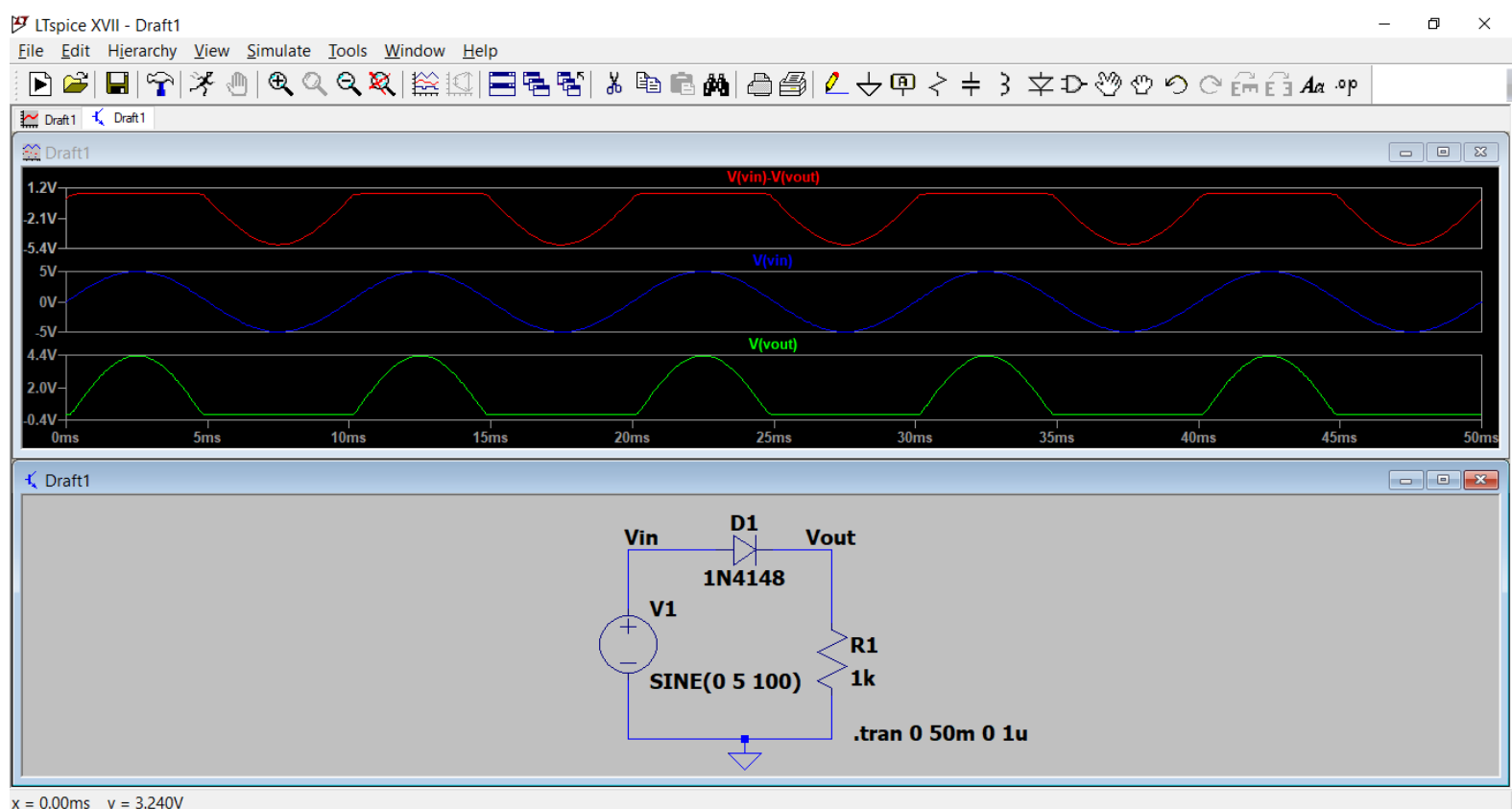


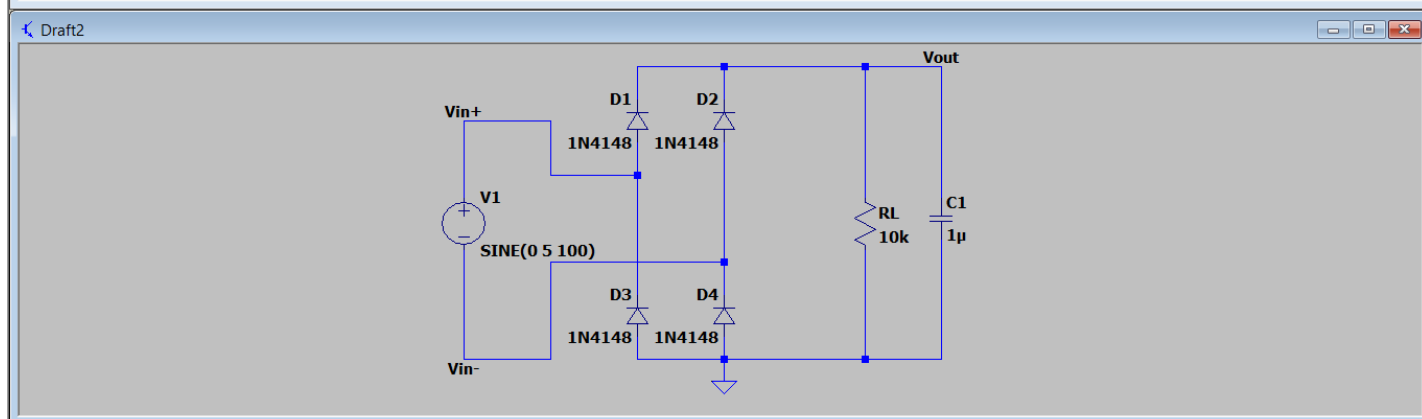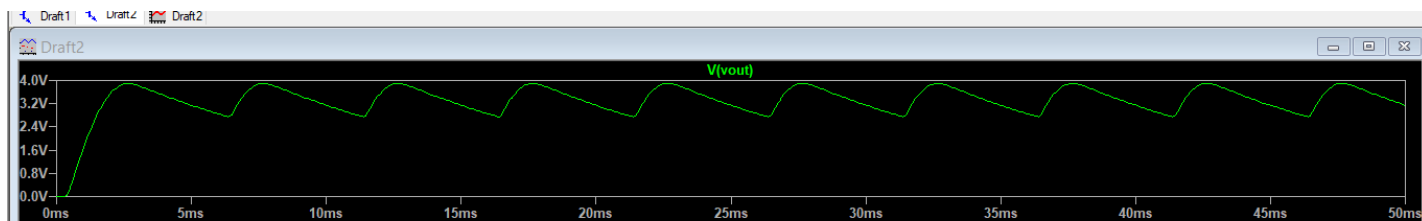

LTspice XVII - Draft2



File Edit Hierarchy View Simulate Tools Window Help


Icons for simulation and editing tools.

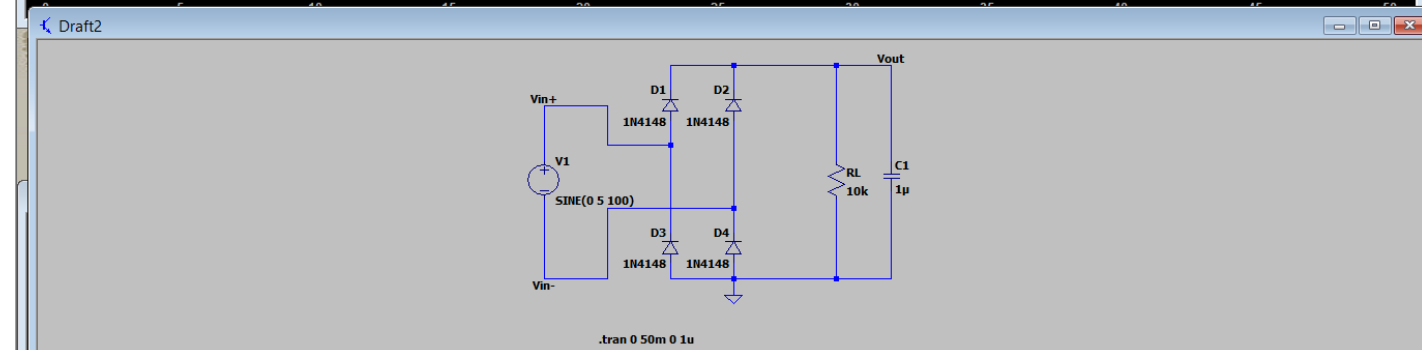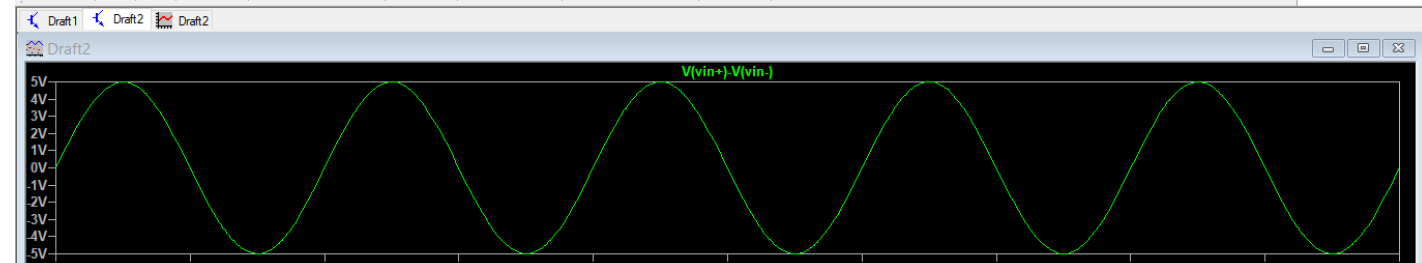


Icons for simulation and editing tools.

Draft2 FW_20301264 HW_20301264

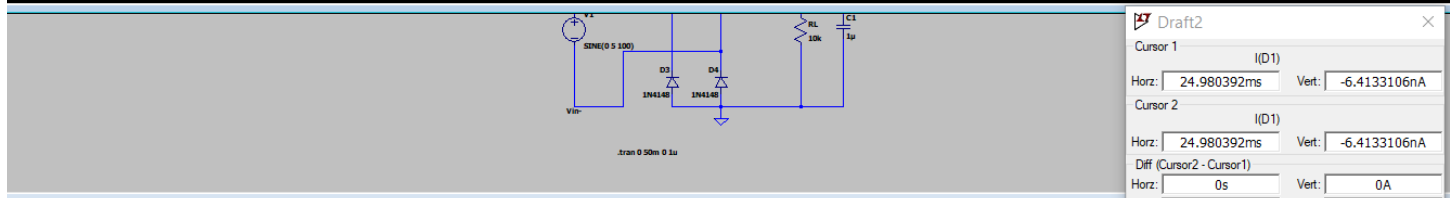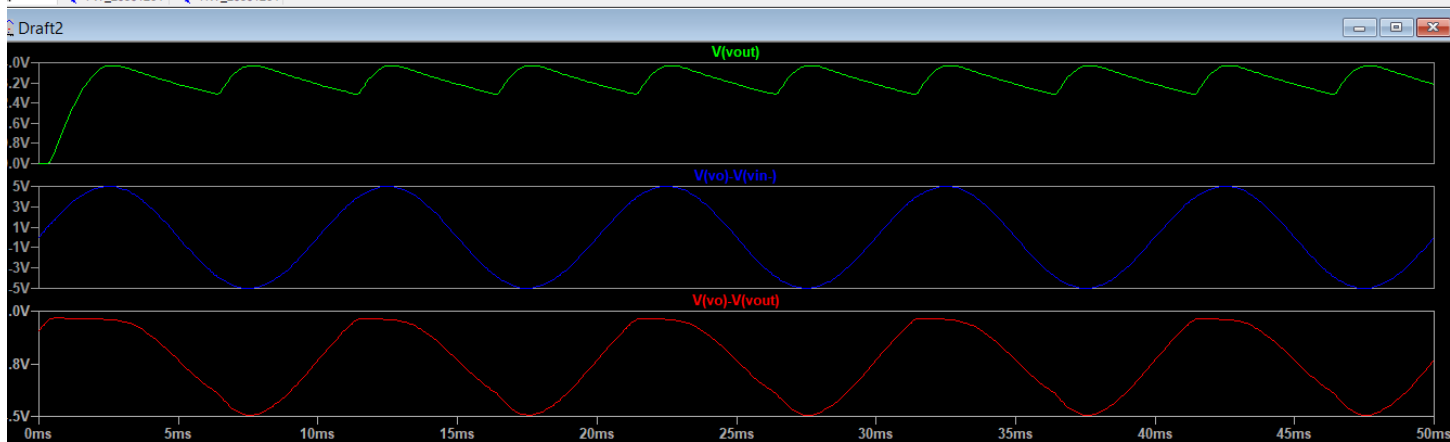

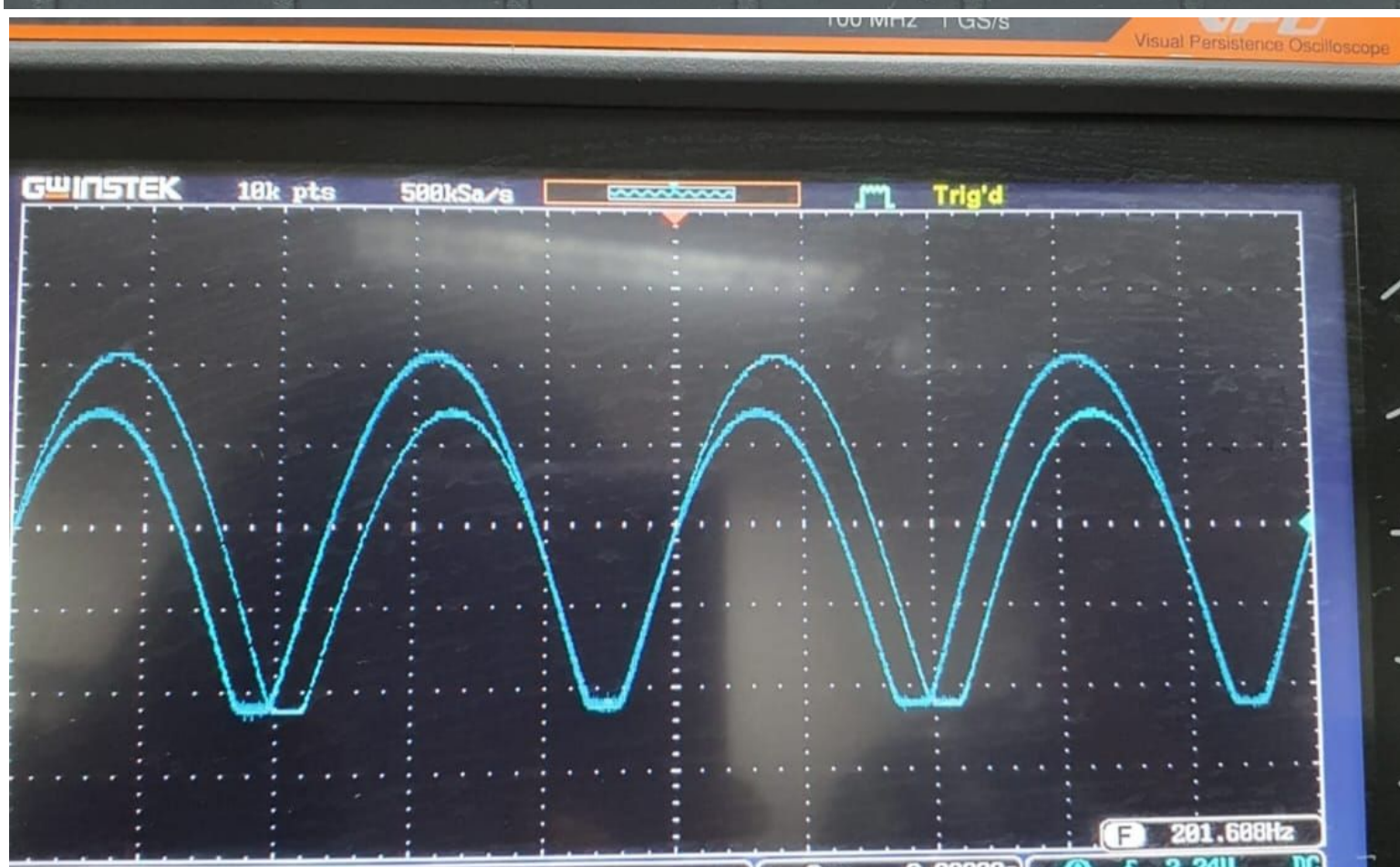

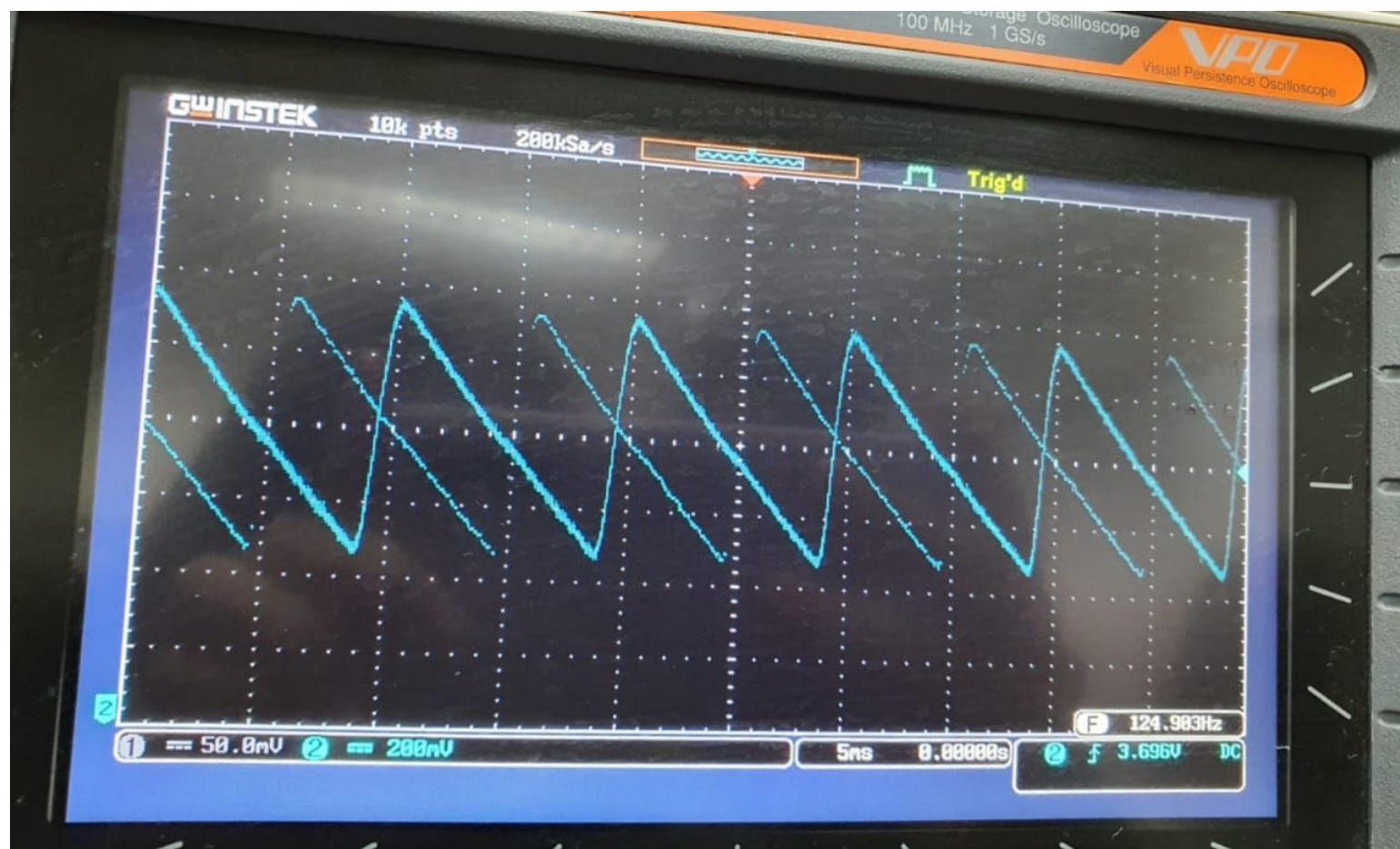

GWINSTEK GDS-1102B

Digital Storage Oscilloscope
100 MHz 1 GS/s

VPO
Video Position Oscilloscope

GWINSTEK

10k pts

200kSa/s

□ 7.68ns
○ 12.5ns
△ 4.98ns
dV/dt 289V/s


① 3.76V

② 4.78V

△ 1.82V

dV/dt 289V/s

Trig'd

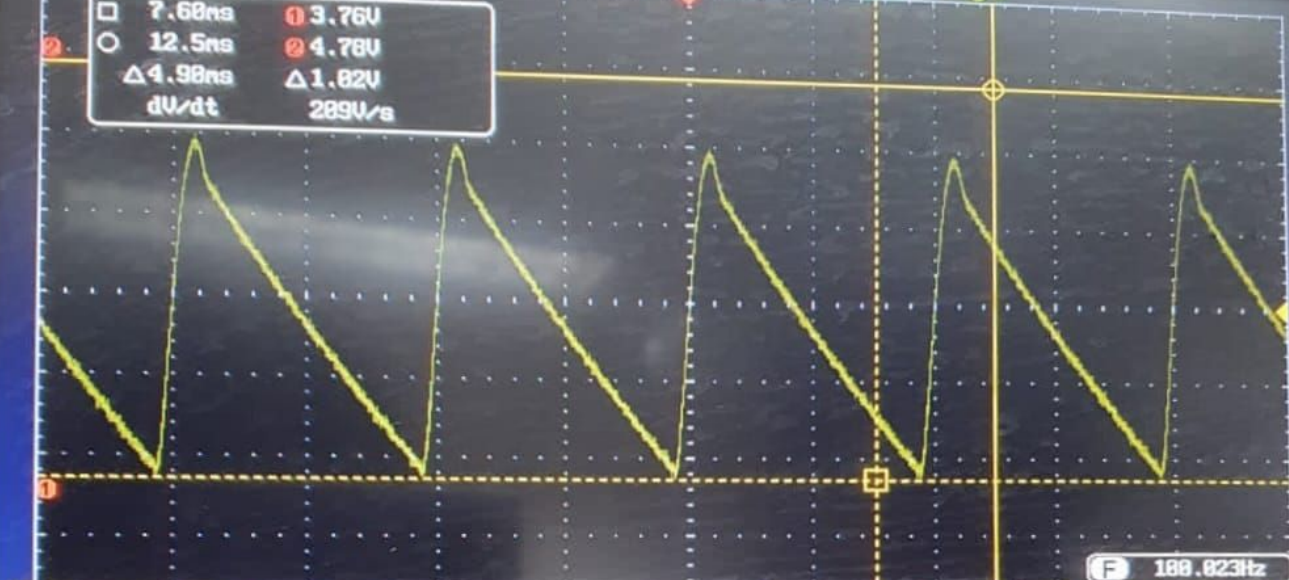

① 200mV ② 5.00V

5ns 8.00000e

① f 4.216V DC

Mode
Fit Screen
AC Priority

Undo
Autoset

~~AD~~ I_{P-P}

$$R = 10.08 \text{ k}\Omega$$

$$V_D = 10.00$$

$$V_{DC} = 328.7 \text{ mV}$$

$$V_{P-P} = 5.36$$

$$V_{RMS} \leftarrow V_{AC} = 3.58 \text{ V}$$

H/W without capacitor

$$V_P = 4.88 \text{ V}$$

$$V_{DC} = 1.866 \text{ V} \rightarrow 1.513 \text{ V}$$

$$V_{RMS} \leftarrow V_{AC} = 1.866$$

H/W with filter capacitor (1 μ F)

$$V_P = 4.84 \text{ V}$$

$$P_H - P_L = 2.56 \text{ V}$$

$$V_{DC} = 3.45 \text{ V}$$

$$V_{RMS} = 0.760 \text{ V}$$

H/W with filter capacitor (4.7 μ F)

$$V_P = 4.68 \text{ V} \rightarrow 4.60 \text{ V}$$

$$P_H - P_L = 1.00 \text{ V}$$

$$V_{DC} = 4.27 \text{ V}$$

$$V_{RMS} = 0.222 \text{ V}$$

FW without capacitors

$$V_p = 4.43 \text{ v}$$

$$P_k - P_k = 4.44 \text{ v}$$

$$V_{DC} = 2.267$$

$$V_{Rms} = 1.374 \text{ v}$$

FW with 1 μ F

$$V_p = 4.34$$

$$P_k - P_k = 1.63$$

$$V_{DC} = 3.376 \text{ v}$$

$$V_{Rms} = 0.401 \text{ v}$$

FW with 4.7 μ F

$$V_p = 4.05 \text{ v}$$

$$V_{DC} = 3.75 \text{ v}$$

$$V_{Rms} = 0.182 \text{ v}$$

$$P_k - P_k = 7.8$$

Dikran
16/10/22

• Which of two rectifier is better?

⇒ I think full wave rectifier is better than half wave rectifier because the average output voltage is higher in full-wave rectifier, also there is less ripple produced in full-wave rectifier when compared to the half-wave rectifier.

• Why can't you see the input and output using 2 channels of oscilloscope simultaneously?

⇒ Usually because an oscilloscope has ground-referenced inputs, and connecting both channels directly would short out portions of the rectifier bridge.

You can certainly make this observation using a scope but you need a scope with floating input channels, or external differential ~~problems~~ probes.

• Challenges during experiment:

⇒ The things that we found challenging while experiment such as, full wave rectifier was harder to implement.

We cannot see input and output at channel 1 and channel 2 at the same time on a oscilloscope for full wave rectifier.