CSE260 Lab Report

Experiment Name: Design a circuit that outputs 2's complement of a 3-bit number using encoder & decoder.

Submitted by

Name: Tahsin Ashrafee Susmit

ID: 20301088

Section: 09


Date: 29/8/2021

1. Name of experiment: Design a circuit that outputs 2's complement of a 3 bit number using encoder 2 decoder.


2. Objective:

- i. To get familianized with using with practical circuits.
- 11. To investigate the output of 2's complement using encoder and decoder
- iii. To get familarized with encoder and decodor.
- 3- Required components and excipments;
 For simulation we need proteous software and
 in proteus software we need;
- 1. Logic Probe (BIG)
- ii. Logic State
- ili. 74 LS138 (Decoder)
- iv. 74 [S148 (Encoder)


4. Experimental Selup:

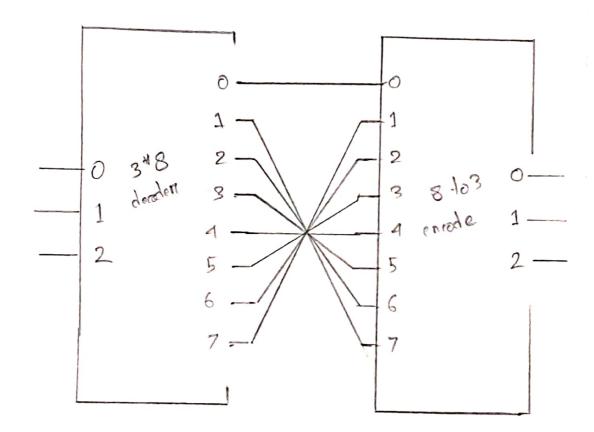

74138 :

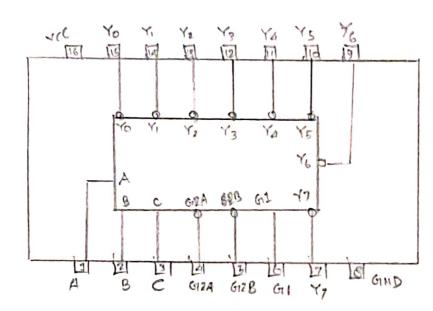

74148;

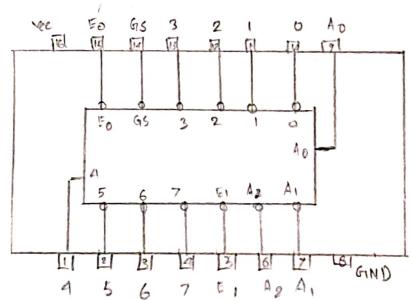


5. Results and Discussions;

| Inputs | | | | out ports | | | | Acetive low | | | output line connection | |
|---------|---|---|---|-----------|----------------|------------|----|----------------|----------------|----------------|------------------------|----------|
| Minterm | С | B | Α | Mintenm | O _z | D , | Do | P ₂ | D ₁ | D _o | Decoden | Encodera |
| 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | ١ | 1 | 1 | 0 | O |
| 1 | 0 | 0 | ı | 7 | ١ | ١ | ١ | 0 | 0 | 0 | ١ | 7 |
| 2 | 0 | ١ | 0 | ζ | 1 | ١ | 0 | 0 | 0 | 1 | 2 | 6 |
| 3 . | 0 | \ | 1 | 5 | 1 | 0 | ١ | 0 | ١ | 0 | 3 | 5 |
| 4 | \ | 0 | 0 | 4 | 1. | 0 | 0 | 0 | ١ | ١ | 4 | 4 |
| 5 | 1 | 0 | 1 | 3 | 0 | 1 | 1 | , | 0 | 0 | 5 | 3 |
| 6 | 1 | 1 | 0 | 2 | 0 | 1 | 0 | \ | 0 | 1 | 6 | 2 |
| 7 | 1 | 1 | 1 | ١ | 0 | 0 | 1 | \ | ı | 0 | 7 | 1 |

The circoil takes a 3 bit value as an import and convents the value to its respective 2's complement for low value by tarper inverting the form of 2's complement.

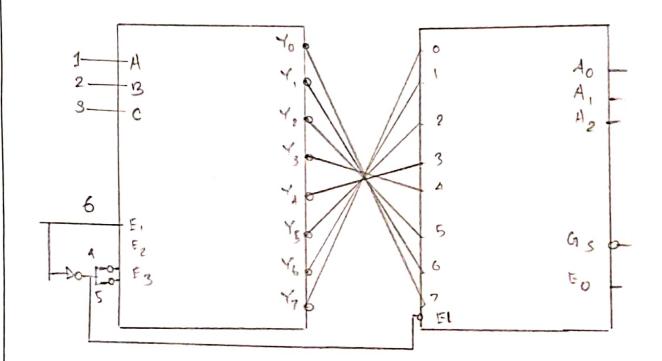(0)

A circuit diagram with encoder and decotor that will output the 1's complement of 3 bit numbers is given below:



(7)

Yes, we can implement a code convention with encoder and decoder. From above, we can see that we can function 1's complement and 2's complement where we could convert one bianary number to another using encoder and decoder. 30, we can say code conversion is possible. We converted 0;0,0 into 11.1 and 0.0,1 to 0,0,0. 30, it is possible.