

# Experiment-02

## Study of Half-Wave and Full-Wave Diode Rectifier Circuit

### CSE251 - Electronic Devices and Circuits Lab

## Objective

1. To build half and full-wave diode rectifier circuit and understand its operating principle.

## Equipments

1. p-n junction diode (1N4007) x 4
2. Resistor ( $10k\Omega$ ) - x1
3. Capacitors ( $1\mu F$ ,  $4.7\mu F$ ) - 1 each
4. Function Generator
5. Oscilloscope
6. Breadboard
7. Chords and Wires

## Background Theory

The diode rectifier converts the input sinusoidal voltage  $V_s$  to a unipolar output  $V_o$ . There are two types of rectifier circuits: (i) Half-wave rectifier and (ii) Full-wave rectifier.

### Half-Wave (HW) Rectifier

The circuit of a half-wave rectifier is shown in the following figure:

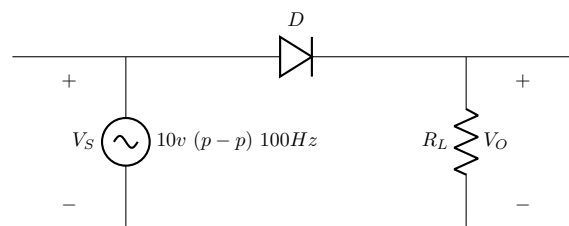


Figure 1: Half-Wave Rectifier

Assuming ideal diode model,

For the period,  $t = 0 \rightarrow T/2$ ,  $V_s > 0$ , Diode is ON and  $V_o = V_s$

For the period,  $t = T/2 \rightarrow T$ ,  $V_s < 0$ , Diode is OFF and  $V_o = 0$

As only positive half cycle appears at the output and the negative half is blocked, the AC input voltage changes into a unidirectional DC voltage at the output. The process of removing half of the input signal to establish a dc level is aptly called half-wave rectification. Due to diode voltage drop, the actual output voltage will be approximately,  $V_o = V_s - V_{D0}$ . For,  $V_s = V_m \sin \omega t$ , DC voltage and current of a half wave rectifier are:

$$V_{DC} = \frac{V_m}{\pi} - \frac{V_{D0}}{2}$$

$$I_{DC} = \frac{V_{DC}}{R} = \frac{V_m/\pi - V_{D0}/2}{R}$$

where,  $V_m$  = peak input voltage,  $V_{D0} \approx 0.7v$  for Si.

The following figures show the input and output wave shapes of a HW rectifier circuit:

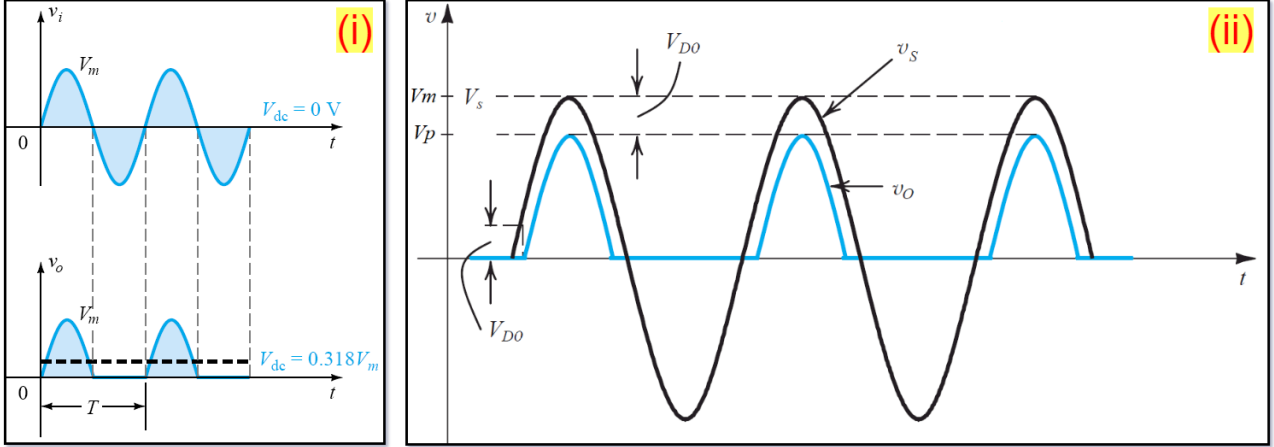


Figure 2: (i) Assuming Ideal Diode (ii) Assuming Real Diode (CVD Model)

### HW Rectifier with Filter Capacitor

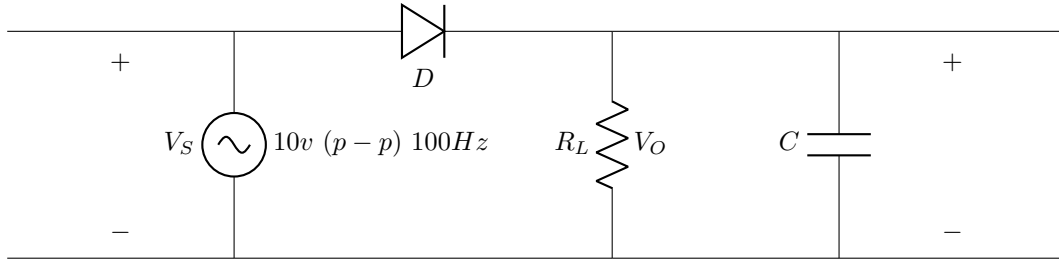


Figure 3: Half-Wave Rectifier with Filter Capacitor

Although the rectification stage makes the sine wave voltage to be positive, the rectifier's result is not as "flat" a DC value as we would like to have from a reliable voltage source, as you will measure in the lab. The capacitor is included to help smooth out the ripples that result in the output from the rectification stage.

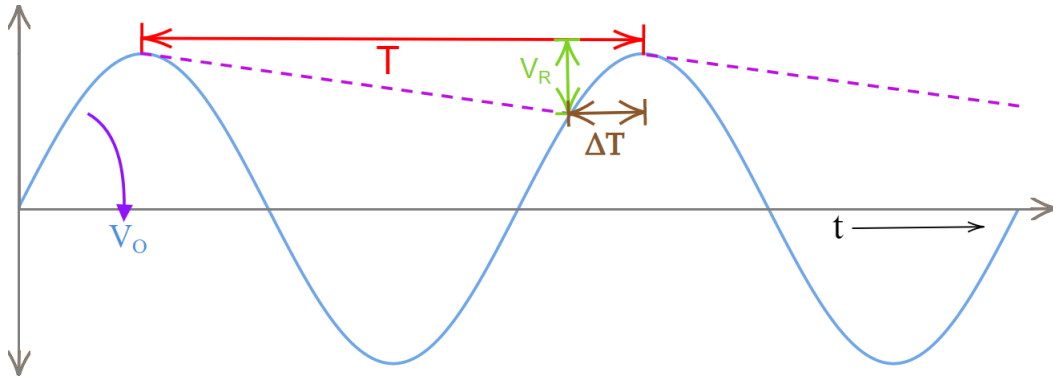


Figure 4:  $V_r$  or  $V_r(p-p)$  is the peak to peak ripple voltage.

Recall that the voltage across a capacitor cannot change instantaneously, but rather it requires a certain amount of time before it is fully charged. Initially, as the input voltage rises, diode turns on, and the capacitor starts charging. After the input voltage reaches its peak value, the capacitor gets charged to the peak input voltage. As the input voltage now starts decreasing below the peak value, the diode turns off, since the n-side is more positive than the p-side due to the voltage across the capacitor which does not change instantaneously. The stored charges on the capacitor will be released through  $R_L$ .

For  $R_L C \gg T$ , it will take long time for the capacitor to discharge and the output terminal will maintain almost a dc voltage. Thus, large capacitance values help suppress the quickly changing voltage from the

rectifier and result in a flatter DC value being supplied to the load. Typical power supply designs use relatively large capacitor values (greater than 1000  $\mu\text{F}$ ).

**Peak Inverse Voltage(PIV):** PIV is the maximum voltage that appears across the diode when it is reverse-biased.

$$PIV = V_m$$

### Ripple Voltage and Ripple Factor

The output of a rectifier though unidirectional, contains periodically fluctuating components. The theoretical value for the peak-to-peak ripple voltage is given by,

$$V_{r(p-p)} = \frac{V_p}{fCR} = \frac{V_m - V_{D0}}{fCR}$$

Here,  $V_p$  = peak voltage of the rectified output,  $f$  = input frequency, and  $R$  is the resistance connected in parallel with  $C$ .

$$\text{Average value of the output wave, } V_{dc} = V_p - \frac{V_{r(p-p)}}{2}$$

$$\text{RMS value of the Ripple Voltage, } V_{r(rms)} = \frac{V_{r(p-p)}}{2\sqrt{3}}$$

A measure of the fluctuating components is given by the ripple factor  $r$ , which is defined as,

$$\begin{aligned} r &= \frac{\text{rms value of alternating components of the output wave (multimeter in AC)}}{\text{average value of the output wave (multimeter in DC)}} \\ &= \frac{V_{r-rms}}{V_{dc}} \end{aligned}$$

### Full-Wave (FW) Rectifier / Bridge Rectifier

The full-wave rectifier utilizes both halves of the input sinusoid. To provide a unipolar output, it inverts the negative halves of the sine wave. Figure-5 shows the circuit diagram, input and output waveform of Full-Wave Rectifier/Bridge Rectifier. In this case, constant voltage drop model was assumed. Peak inverse voltage across

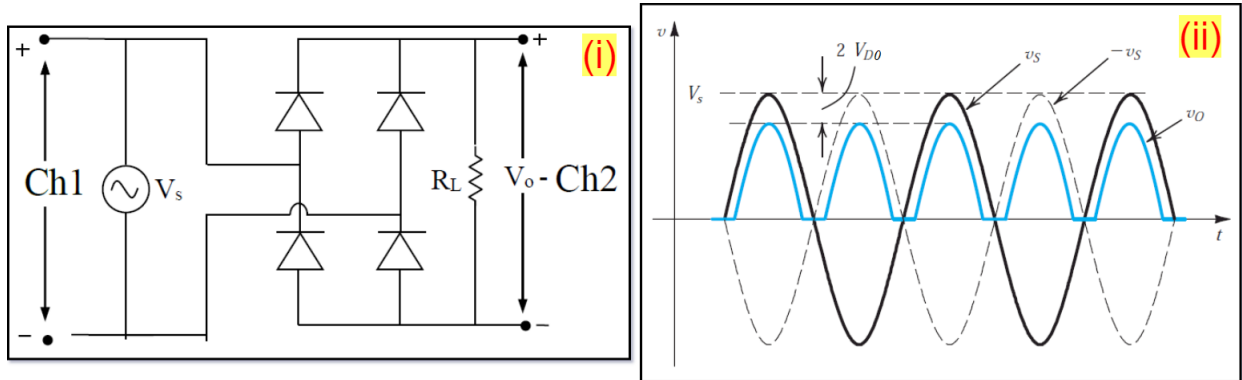


Figure 5: (i) Full-Wave Rectifier Circuit without Capacitor (ii) Input and Output Waveform

each diode and DC voltage in reverse-bias can be calculated using the following equations,

$$PIV = V_m - V_{D0}$$

$$V_{DC} = \frac{2V_m}{\pi} - 2V_{D0}$$

## Full-Wave (FW) Rectifier with Capacitor

The pulsating nature of the output voltage produced by the rectifier circuits discussed above makes it unsuitable as a dc supply for electronic circuits. A simple way to reduce the variation of the output voltage is to place a capacitor across the load resistor. Figure-6 shows the circuit diagram and output waveform of Full-Wave Rectifier with Capacitor.

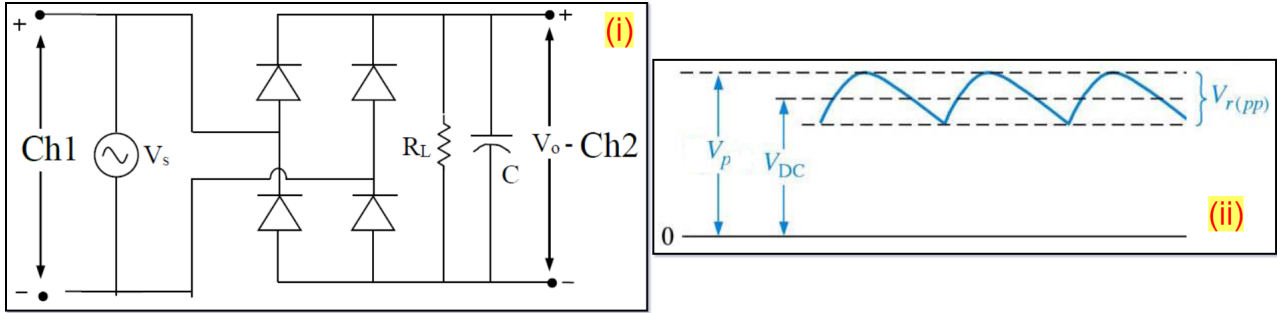


Figure 6: (i) Full-Wave Rectifier Circuit with Capacitor (ii) Output Waveform

### Ripple Voltage and Ripple Factor

The output of a rectifier though unidirectional, contains periodically fluctuating components. The theoretical value for the peak-to-peak ripple voltage is given by,

$$V_{r(p-p)} = \frac{V_p}{2fCR} = \frac{V_m - 2V_{D0}}{2fCR}, \text{ for a FW rectifier circuit}$$

Here,  $V_p$  = peak voltage of the rectified output,  $f$  = input frequency, and  $R$  is the resistance connected in parallel with  $C$ .

$$\text{Average value of the output wave, } V_{dc} = V_p - \frac{V_{r(p-p)}}{2}$$

$$\text{RMS value of the Ripple Voltage, } V_{r-rms} = \frac{V_{r(p-p)}}{2\sqrt{3}}$$

A measure of the fluctuating components is given by the ripple factor  $r$ , which is defined as

$$r = \frac{\text{rms value of alternating components of the output wave (multimeter in AC)}}{\text{average value of the output wave (multimeter in DC)}}$$

$$= \frac{V_{r-rms}}{V_{dc}}$$

## Task-01: HW Rectifier

### Procedure

1. Construct circuit of Figure 1. Observe  $V_s$  and  $V_o$  simultaneously on Channel 1 and Channel 2 of the oscilloscope respectively.
2. Save the input and output waveforms in your memory stick, or sketch the waveforms on a tracing paper.
3. Measure  $V_o$  with a multimeter in dc and ac mode.
4. Connect  $1\mu\text{F}$  capacitor across the load resistor,  $R_L$  (**Be careful** about the polarity of the capacitor).
5. Save the output waveform in your memory stick, or sketch the waveform on a tracing paper.
6. Measure the peak voltage of the output,  $V_p$  and peak-to-peak ripple voltage  $V_{r(p-p)}$  from the oscilloscope (To measure the peak and the ripple voltages, go to the "measure" tab of the oscilloscope or switch on the cursors of the oscilloscope. This allows you to level your cursor horizontally with the peak or the ripple voltage and measure the values).
7. Also measure  $V_o$  with a multimeter in dc and ac mode and calculate the ripple factor.
8. Replace  $1\mu\text{F}$  Capacitor with  $4.7\mu\text{F}$  and repeat steps 4-7.

## Experimental Observation

### 1. HW Rectifier without Capacitor:

Peak output voltage,  $V_p$  (oscilloscope) =

Average or DC output voltage,  $V_{dc}$  (multimeter in DC mode) =

RMS or AC output voltage,  $V_{r-rms}$  (multimeter in AC mode) =

### 2. HW Rectifier with $1\mu\text{F}$ Capacitor:

Peak output voltage,  $V_p$  (oscilloscope) =

Peak to peak ripple voltage,  $V_{r(p-p)}$  (oscilloscope) =

Average or DC value of the ripple voltage,  $V_{dc}$  (multimeter in DC mode) =

RMS or AC value of the ripple voltage,  $V_{r-rms}$  (multimeter in AC mode) =

Ripple factor,  $r = V_{r-rms}/V_{dc}$  =

### 3. HW Rectifier with $4.7\mu\text{F}$ Capacitor:

Peak output voltage,  $V_p$  (oscilloscope) =

Peak to peak ripple voltage,  $V_{r(p-p)}$  (oscilloscope) =

Average or DC value of the ripple voltage,  $V_{dc}$  (multimeter in DC mode) =

RMS or AC value of the ripple voltage,  $V_{r-rms}$  (multimeter in AC mode) =

Ripple factor,  $r = V_{r-rms}/V_{dc}$  =

## Theoretical Calculation (Homework)

### 1. HW Rectifier Without Capacitor:

Peak output voltage,  $V_p$  (see the experimental observation) =

Peak input voltage,  $V_m$  =

Diode voltage,  $V_{D0} = 0.7\text{ V}$

DC output voltage of the rectifier,  $V_{dc} = \frac{V_m}{\pi} - \frac{V_{D0}}{2}$  =

RMS or AC output voltage,  $V_{r-rms} = \frac{V_p}{2}$  =

### 2. HW Rectifier With $1\mu\text{F}$ Capacitor:

Peak output voltage,  $V_p$  (see the experimental observation) =

Peak to peak ripple voltage,  $V_{r(p-p)}$  (see the experimental observation) =

DC value of the ripple voltage,  $V_{dc} = V_p - \frac{V_{r(p-p)}}{2}$  =

RMS value of the ripple voltage,  $V_{r-rms} = \frac{V_{r(p-p)}}{2\sqrt{3}}$  =

Ripple factor,  $r = V_{r-rms}/V_{dc}$  =

### 3. HW Rectifier with $4.7\mu\text{F}$ Capacitor:

Peak output voltage,  $V_p$  (see the experimental observation) =

Peak to peak ripple voltage,  $V_{r(p-p)}$  (see the experimental observation) =

DC value of the ripple voltage,  $V_{dc} = V_p - \frac{V_{r(p-p)}}{2}$  =

RMS value of the ripple voltage,  $V_{r-rms} = \frac{V_{r(p-p)}}{2\sqrt{3}}$  =

Ripple factor,  $r = V_{r-rms}/V_{dc}$  =

## Task-02: FW Rectifier

---

### Procedure

1. Construct circuit of Figure 6 without the capacitor. Observe  $V_s$  and  $V_o$  separately on the oscilloscope [i.e use only one channel].
2. Save the input and output waveforms in your memory stick, or sketch the waveforms on a tracing paper.
3. Measure  $V_o$  with a multimeter in dc and ac mode.
4. Connect  $1\mu\text{F}$  capacitor across the load resistor,  $R_L$  (BE CAREFUL about the polarity of the capacitor).
5. Save the output waveform in your memory stick, or sketch the waveform on a tracing paper.
6. Measure the peak voltage of the output,  $V_p$  and peak-to-peak ripple voltage  $V_{r(p-p)}$  from the oscilloscope (To measure the peak and the ripple voltages, go to the "measure" tab of the oscilloscope or switch on the cursors of the oscilloscope. This allows you to level your cursor horizontally with the peak or the ripple voltage and measure the values).

7. Also measure  $V_o$  with a multimeter in dc and ac mode and calculate the ripple factor.
8. Replace  $1\mu\text{F}$  Capacitor with  $4.7\mu\text{F}$  and repeat steps 4-7.

## Experimental Observation

### 1. FW Rectifier without Capacitor:

Peak output voltage,  $V_p$  (oscilloscope) =  
 Average or DC output voltage,  $V_{dc}$  (multimeter in DC mode) =  
 RMS or AC output voltage,  $V_{r-rms}$  (multimeter in AC mode) =

### 2. FW Rectifier with $1\mu\text{F}$ Capacitor:

Peak output voltage,  $V_p$  (oscilloscope) =  
 Peak to peak ripple voltage,  $V_{r(p-p)}$  (oscilloscope) =  
 Average or DC value of the ripple voltage,  $V_{dc}$  (multimeter in DC mode) =  
 RMS or AC value of the ripple voltage,  $V_{r-rms}$  (multimeter in AC mode) =  
 Ripple factor,  $r = V_{r-rms}/V_{dc} =$

### 3. FW Rectifier with $4.7\mu\text{F}$ Capacitor:

Peak output voltage,  $V_p$  (oscilloscope) =  
 Peak to peak ripple voltage,  $V_{r(p-p)}$  (oscilloscope) =  
 Average or DC value of the ripple voltage,  $V_{dc}$  (multimeter in DC mode) =  
 RMS or AC value of the ripple voltage,  $V_{r-rms}$  (multimeter in AC mode) =  
 Ripple factor,  $r = V_{r-rms}/V_{dc} =$

## Theoretical Calculation (Homework)

### 1. FW Rectifier without Capacitor:

Peak output voltage,  $V_p$  (see the experimental observation) =  
 Peak input voltage,  $V_m =$   
 Diode voltage,  $V_{D0} = 0.7 \text{ V}$   
 DC output voltage of the rectifier,  $V_{dc} = \frac{2}{\pi} V_m - 2 V_{D0} =$   
 RMS or AC output voltage,  $V_{r-rms} = \frac{V_p}{\sqrt{2}} =$

### 2. FW Rectifier with $1\mu\text{F}$ Capacitor:

Peak output voltage,  $V_p$  (see the experimental observation) =  
 Peak to peak ripple voltage,  $V_{r(p-p)}$  (see the experimental observation) =  
 DC value of the ripple voltage,  $V_{dc} = V_p - \frac{V_{r(p-p)}}{2} =$   
 RMS value of the ripple voltage,  $V_{r-rms} = \frac{V_{r(p-p)}}{2\sqrt{3}} =$   
 Ripple factor,  $r = V_{r-rms}/V_{dc} =$

### 3. FW Rectifier with $4.7\mu\text{F}$ Capacitor:


Peak output voltage,  $V_p$  (see the experimental observation) =  
 Peak to peak ripple voltage,  $V_p$  (see the experimental observation) =  
 DC value of the ripple voltage,  $V_{dc} = V_p - \frac{V_{r(p-p)}}{2} =$   
 RMS value of the ripple voltage,  $V_{r-rms} = \frac{V_{r(p-p)}}{2\sqrt{3}} =$   
 Ripple factor,  $r = V_{r-rms}/V_{dc} =$

## Task-03: Simulation (Homework)


In this task, we will simulate the experiment in LTspice and verify the results that were obtained in Hardware lab. We will use transient analysis to simulate a HW and a FW rectifier circuit and study the waveforms. Follow the instructions of following section to perform the simulation.

### HW Rectifier

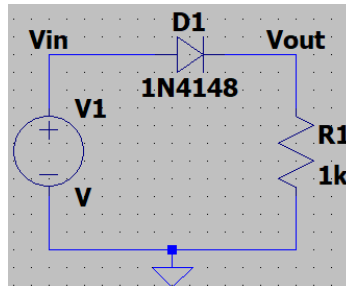
1. Open a new schematic, build the circuit of a HW Rectifier, Save the file using: "HW\_Your ID.asc".
2. Select the diode model as '1N4148' and label the nodes as shown in the following figure.



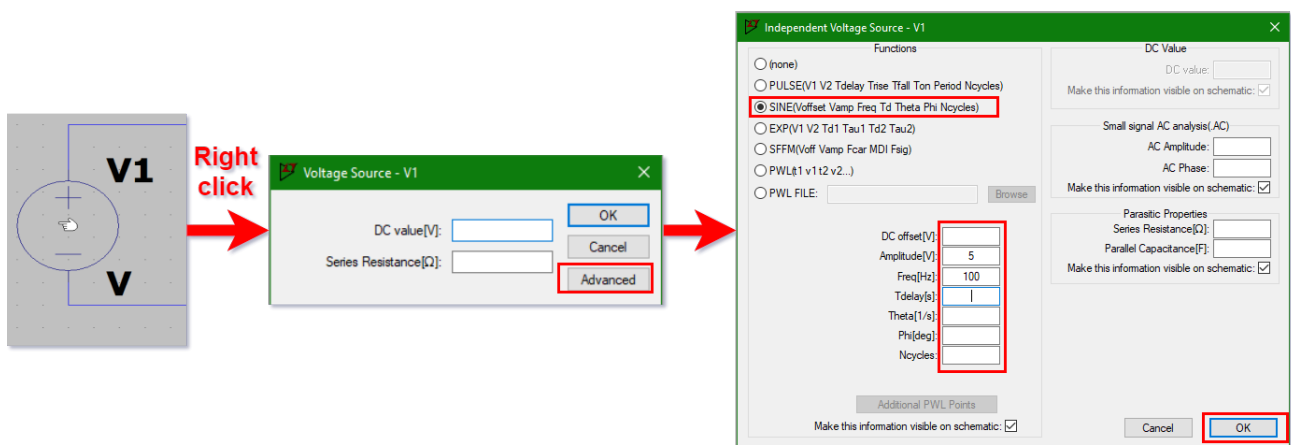3. A sinusoidal ac voltage will be applied to the rectifier circuit to study its behaviour. Go to the properties of the voltage source by Right clicking on it → Advanced. This will launch the property editor, as shown below. Configure the properties as seen in the next figure.



4. Go to 'Edit Simulation Command' window. In the transient tab, set the 'Stop time' as 50 ms with a 'Maximum Timestep' 1  $\mu$ s. Leave the remaining fields unchanged.

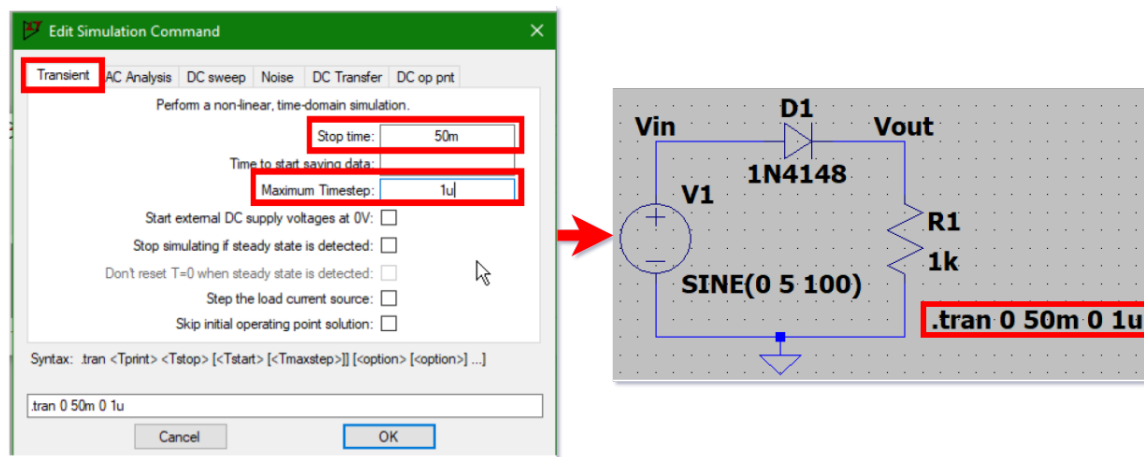

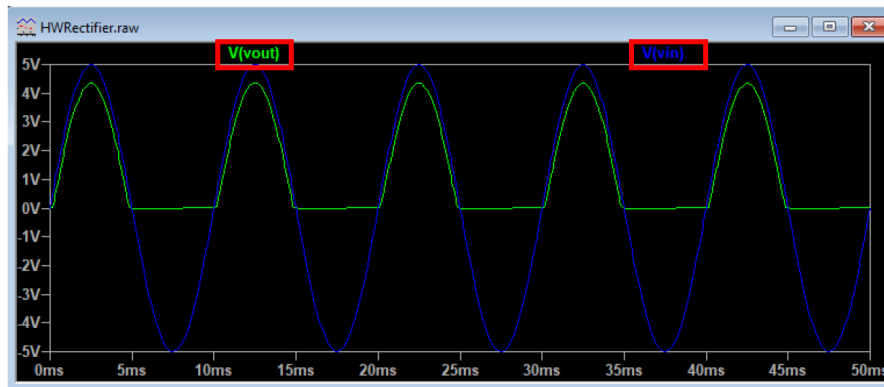


Figure 7: Step-5

5. Run the simulation. Plot Vout. Repeat the same process to plot Vin in the same plot window.
6. To delete a particular trace, hover the cursor on the parameter → Right click → Delete this Trace.

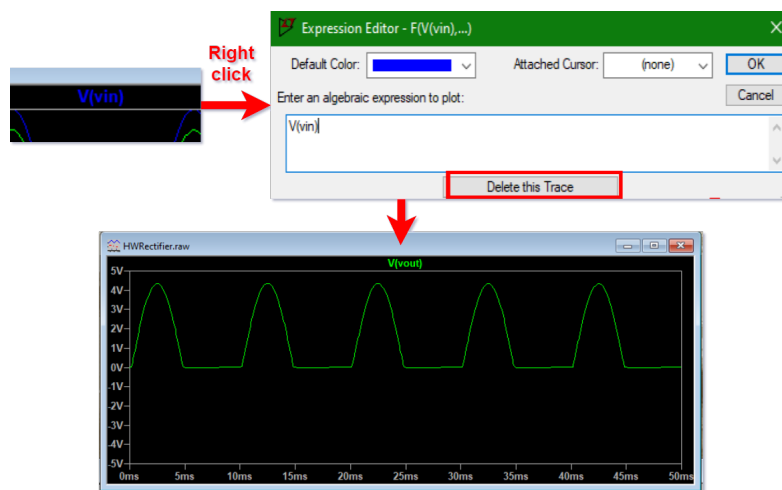


Figure 8: Step-6

7. Multiple plot panes can be added to separately plot different circuit parameters. Right click on the black area → Add Plot Pane. The plot window will now have a new pane. If necessary, adjust the size of the plot window by extending it from the boundary or maximizing it. Currents/voltages can be plotted to each pane. To delete a specific pane, Right-click it → Delete this Pane.

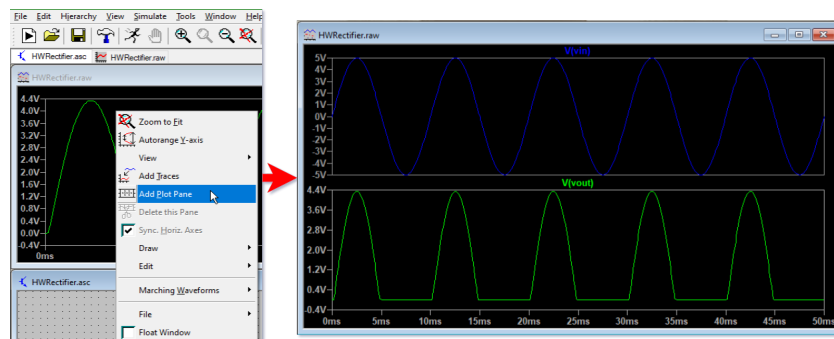


Figure 9: Step-7

8. To see the voltage across the diode, Right click on the black area → Add trace → write  $V(b) - V(c)$  in the 'Expression(s) to add field' of the Trace adding window and hit OK. Note that the maximum reverse bias voltage (Peak Inverse Voltage) across the diode is 5 V.



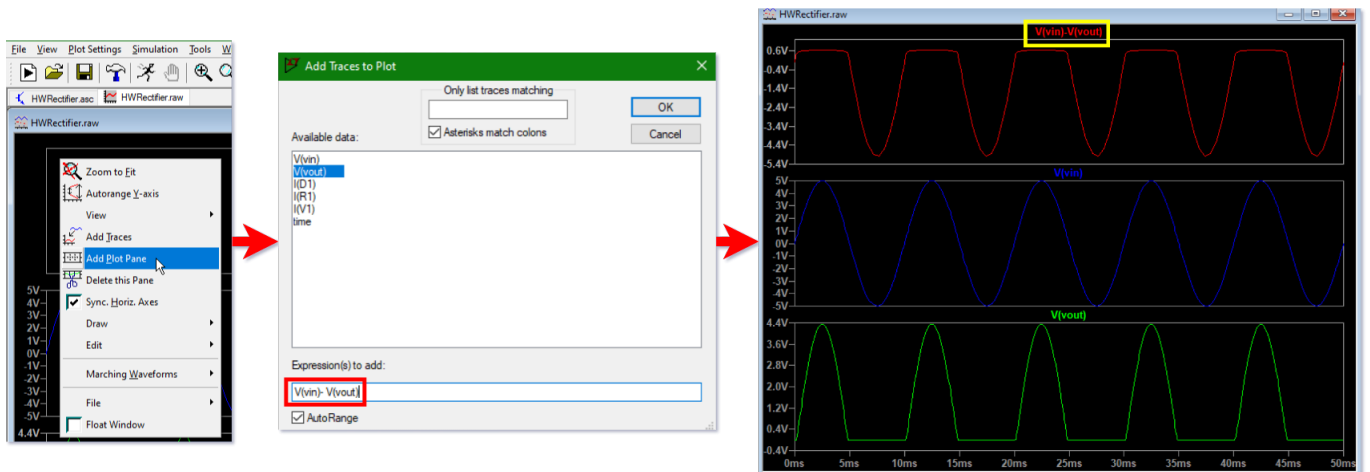


Figure 10: Step-8

9. Add a capacitor of  $1\mu F$  in parallel to the resistor. Change the resistance of the circuit to 10k to increase the time constant.

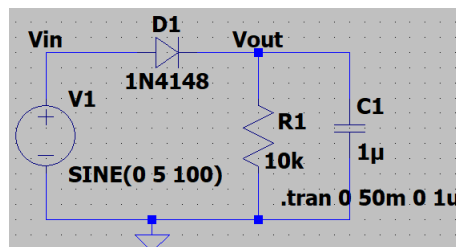


Figure 11: Step-9

10. Run again and observe the waveforms. Further increase in resistance or capacitance will make the output voltage more flatten.

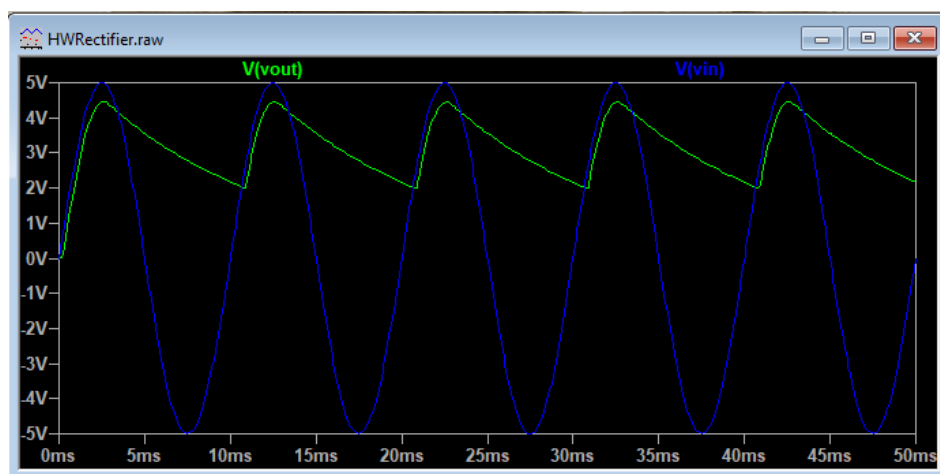


Figure 12: Step-10

## FW Rectifier

- Follow the instructions from the simulation of HW Rectifier and simulate the FW Rectifier with  $R = 10k\Omega$  and  $C = 1\mu F$ . Use the following figure as your starting point and Build the circuit accordingly.

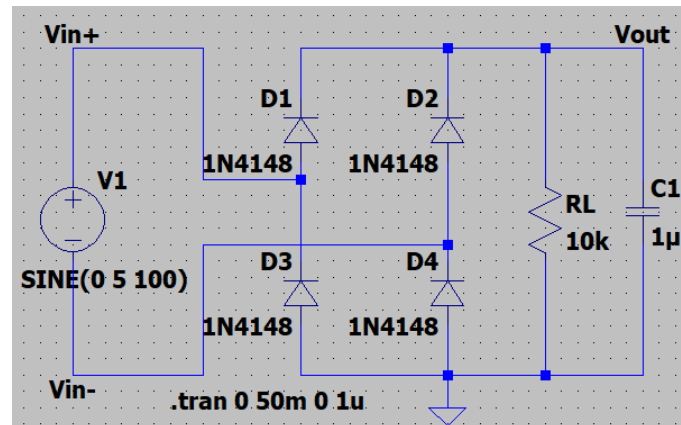


Figure 13: FW Rectifier Schematic

- Plot 'Vout'. Take screenshot.
- Plot 'V1 = Vin+ - Vin-' and take screenshot.
- Plot the voltage across the diode D1. Take screenshot.
- Plot all the things mentioned above in a single graph and take screenshot.

## Task-04: Report

- Cover page [include course code, course title, name, student ID, group, semester, date of performance, date of submission]
- Calculate the average and effective (RMS) values of the load voltages of HW and FW rectifiers without capacitor [see homeworks]. Compare these values with those obtained with the multimeter.
- Calculate the ripple factor for the HW and FW rectifiers [see homeworks] and complete the following table. Compare your results with the calculated values.

	C(uF)	Experimental Observation			Theoretical Calculation		
		Vr-rms (V)	Vdc (V)	Ripple Factor	Vr-rms (V)	Vdc (V)	Ripple Factor
HW	1						
	4.7						
FW	1						
	4.7						

- Circuit diagrams of HW and FW rectifier circuits
- Saved images/traces of the waveforms.
- Signed data sheet/calculation.
- Simulation Part:** Attach the schematic diagrams of HW and FW Rectifier. Also, attach all the screenshots taken in the simulation part.
- The report should have a **Discussion** part. Discussion should contain the answers of the following questions:
  - Which capacitor acts as a better filter? Explain your answer.
  - Which of the two rectifiers is better? Explain why.
  - Why can't you see the input and output using 2 channels of oscilloscope simultaneously?
  - Challenges during the experiment