

CSE260 Lab Report

Experiment Name: Implementation of 4-bit Magnitude Comparator

Submitted by

Name: Tahsin Ashrafee Susmit

ID: 20301088

Section: 09

Date: 11/9/2021

1. Name of the Experiment: Implementation of 4-bit Magnitude Comparator

2. Objective:

- i. To implement 4-bit magnitude comparator
- ii. To implement the circuit (for two 4-bit numbers)
- iii. To gain knowledge about 4-bit magnitude comparator.


3. Required components:

For simulation we need proteus software and in it we require:

- i. Logic Probe (Big)
- ii. Logic State
- iii. 7485

4. Experimental Setup:

A_3 A_2 A_1 A_0 B_3 B_2 B_1 B_0

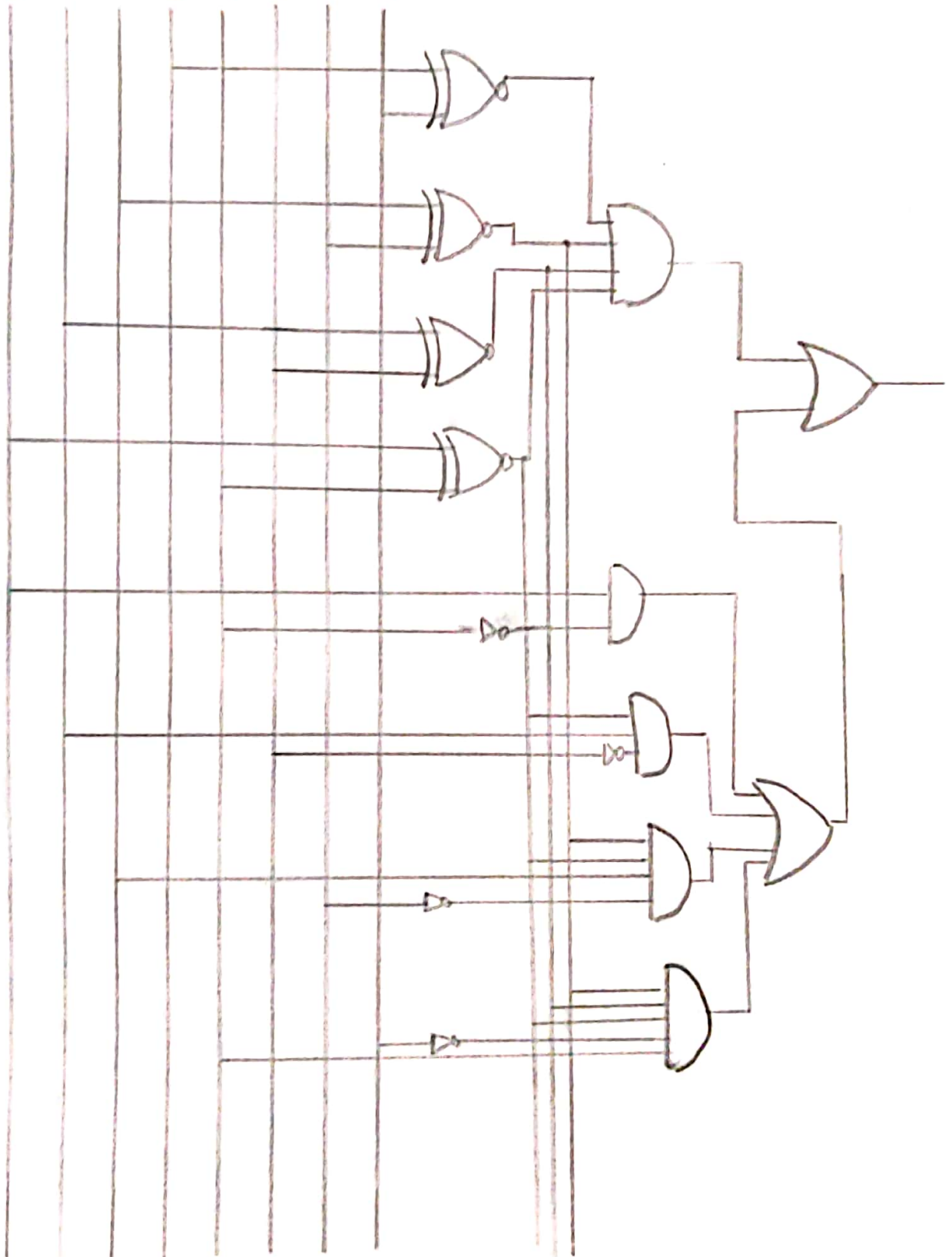

5. Result and Discussions:

(a) $A = B : (I)$;

$$A_0 = B_0 \text{ and } A_1 = B_1 \text{ and } A_2 = B_2 \text{ and } A_3 = B_3$$

$$A = B = (A_3 B_3' + A_3' B_3)' \cdot (A_2 B_2' + A_2' B_2)' \cdot (A_1 B_1' + A_1' B_1)' \cdot (A_0 B_0' + A_0' B_0)'$$

$$\therefore A = B = x_3 \cdot x_2 \cdot x_1 \cdot x_0$$

(b) $A > B : (J)$;

$$A_3 = 1 \text{ and } B_3 = 0 \text{ } A_3 \cdot B_3' \text{ or } (A_3 = B_3) \text{ and } (A_2 = B_2) \text{ and } (A_1 = B_1) \text{ and } (A_0 = 1 \text{ and } B_0 = 0) x_3 x_2 x_1 A_0 B_0'$$

(c) $A < B : (K)$

$$A_3 = 0 \text{ and } B_3 = 1, A_3 B_3 \text{ or } (A_3 = B_3) \text{ and } (A_2 = 0 \text{ and } B_2 = 1) : x_3 x_2' A_2' B_2 \text{ or } (A_3 = B_3) \text{ and } (A_2 = B_2) \text{ and } (A_1 = 0 \text{ and } B_1 = 1) : x_3 x_2 \cdot A_1' B_1 \text{ or } (A_3 = B_3) \text{ and } (A_2 = B_2) \text{ and } (A_1 = B_1) \text{ and } (A_0 = 0 \text{ and } B_0 = 1) : x_3 x_2 x_1 A_0' B_0$$

The changes we need to make:

$$A = B : (I) = \pi_0 \pi_1 \pi_2 \pi_3$$

$$A > B : (J) = A_3 B_3' + \pi_3 A_2 B_2' + \pi_3 \pi_2 A_1 B_1' + \pi_3 \pi_2 \pi_1 A_0 B_0'$$

$$A < B : (K) = A_3' B_3 + \pi_3 A_2' B_2 + \pi_3 \pi_2 A_1 B_1' + \pi_3 \pi_2 \pi_1 A_0' B_0$$

For $(A < B)$

$(A < B)$ if A is not equal to B and A is greater than B

$$\therefore (A < B) = I' \cdot J'$$

$$K = (I + J)'$$

Implementation using NOR-gate:

$A > B$	$A = B$	$A < B$
0	0	1
0	1	0
1	0	0
1	1	undefined